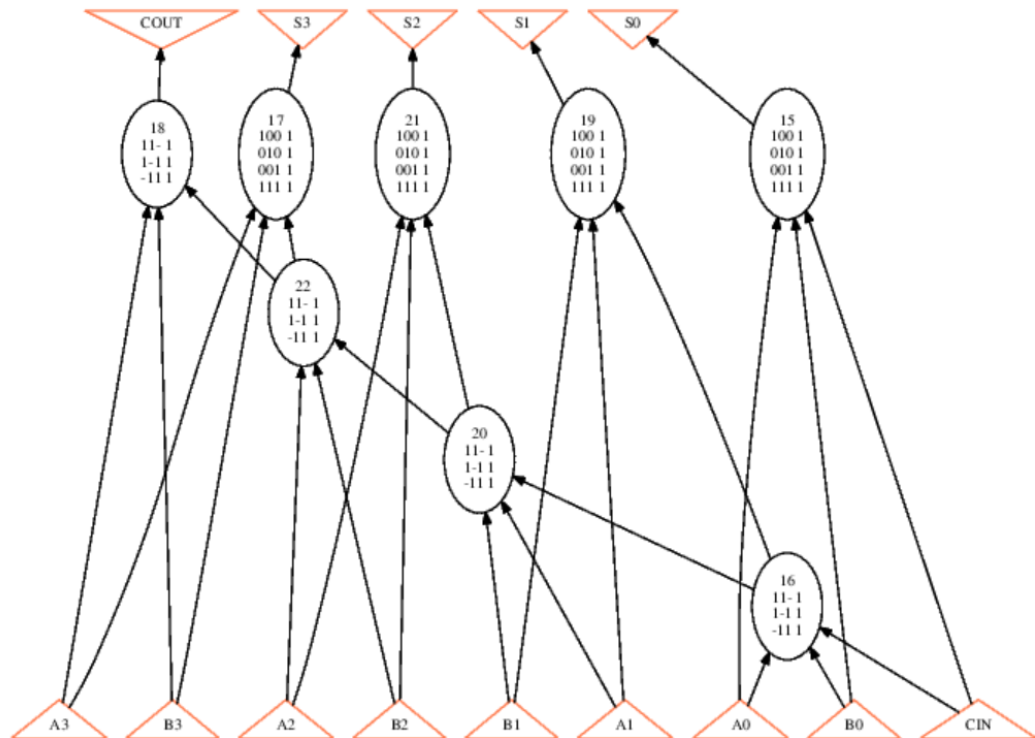



1. Show

Network structure visualized by ABC
Benchmark "4bitadder". Time was Tue Oct 13 19:35:03 2020.

The network contains 8 logic nodes and 0 latches.



2. Strash -> show

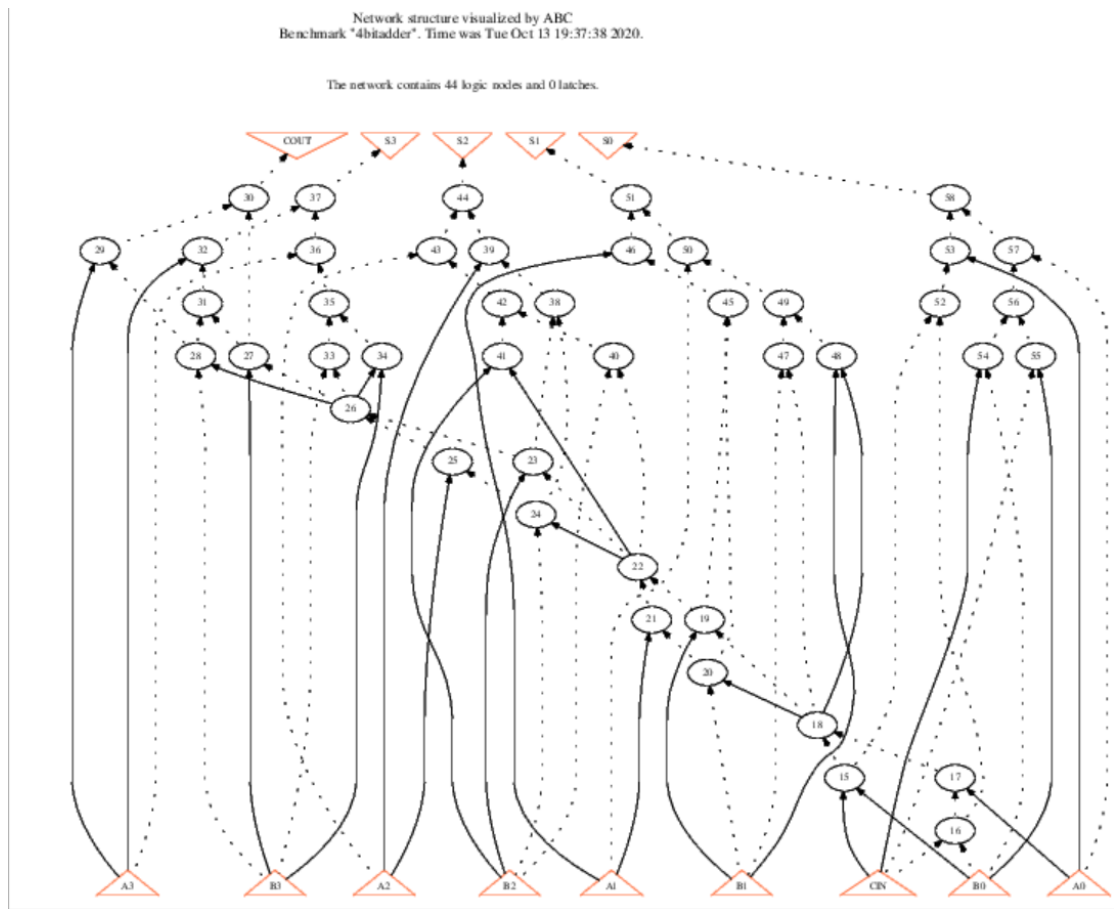

3. show_bdd

