


**PART 1**

(a) The blif file is named 4bitadder.blif and put in the same directory.

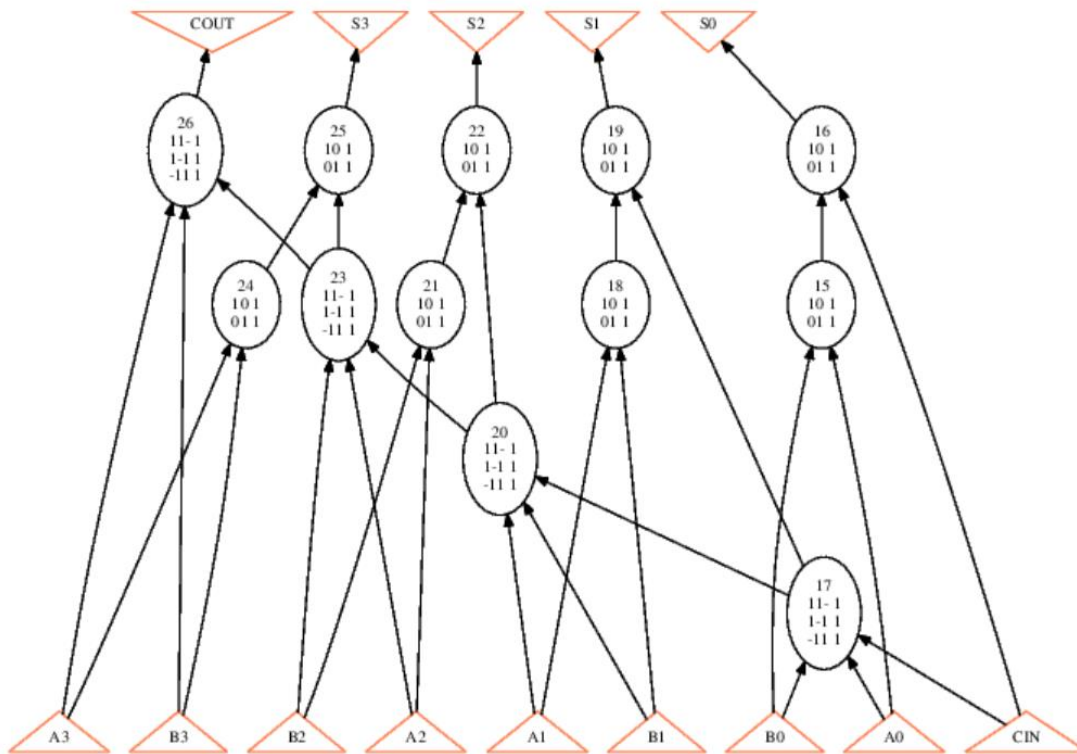(b) Results of show and show\_bdd:


Step 3. (show)

The network contains 12 logic nodes and 0 latches.




Step 5.(show, after strash)

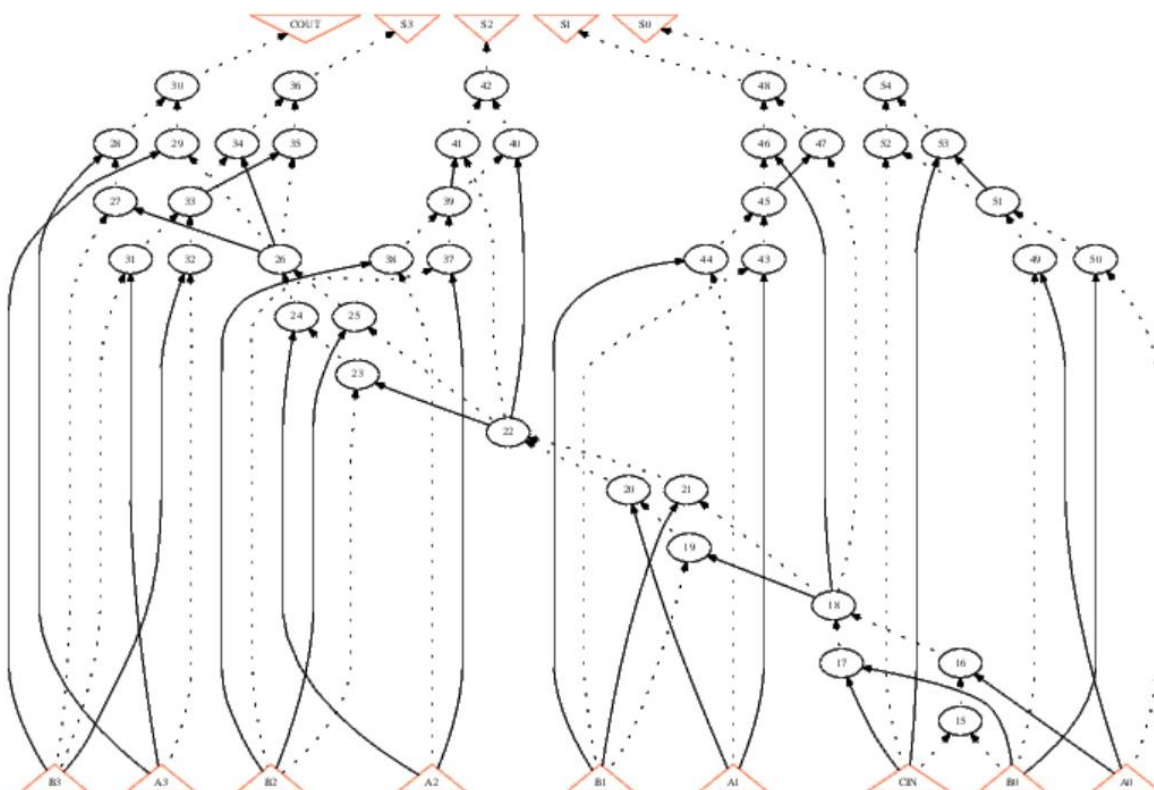The network contains 40 logic nodes and 0 latches.



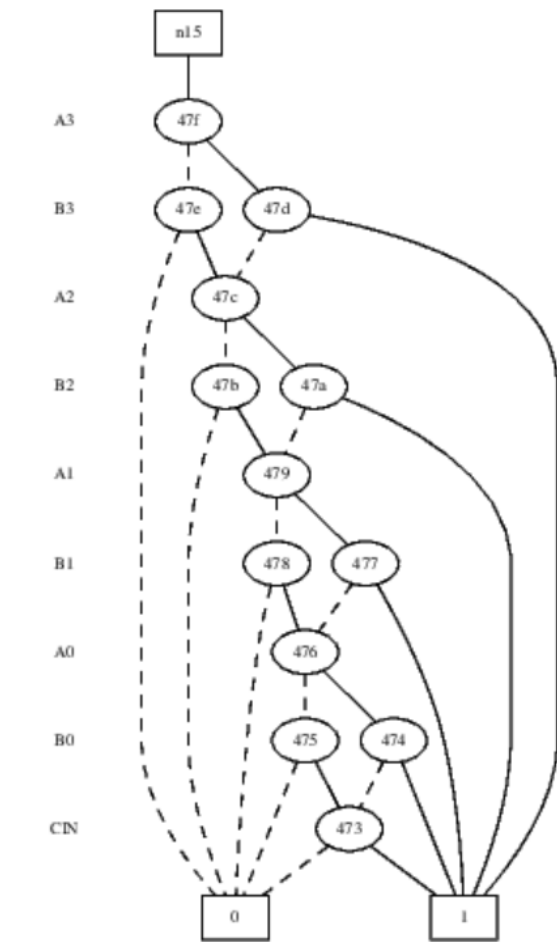Step 7.(show\_bdd, it's the result of the first PO, COUT.)



## PART 2

(a1) logic network in AIG vs. structurally hashed AIG

command “aig” : converts node functions to AIG.

command “strash”: Do structural hashing and transform combinational logic into an AIG.

Take 4-bit full adder as an example, show the status by command “print\_stats”:

```
abc 07> read 4bitadder.blif
Hierarchy reader flattened 4 instances of logic boxes and left 0 black boxes.
abc 08> aig
abc 08> print_stats
4bitadder          : i/o =   9/   5  lat =   0  nd =   12  edge =   28  aig =   40  lev =  4
abc 08> strash
abc 09> print_stats
4bitadder          : i/o =   9/   5  lat =   0  and =   40  lev = 12
abc 09>
```

(a2)

```
abc 13> read 4bitadder.blif
Hierarchy reader flattened 4 instances of logic boxes and left 0 black boxes.
abc 14> bdd
abc 14> print_stats
4bitadder          : i/o =   9/   5  lat =   0  nd =   12  edge =   28  bdd =   32  lev =  4
abc 14> collapse
abc 15> print_stats
4bitadder          : i/o =   9/   5  lat =   0  nd =    5  edge =   33  bdd =   43  lev =  1
abc 15>
```

command “bdd”: converts node functions to bdd.

command “collapse”: collapses the network by constructing global BDD.

Take 4-bit full adder as an example, command “collapse” constructs global function to BDD. (global function: inputs=A0,A1,A2,A3,B0,B1,B2,B3,CIN. output=COUT,s0,s1,s2,s3) While command “bdd” constructs local function to BDD. (local function: inputs=a, b, cin. output=s, cout)

(b) command “logic” can transform an AIG into logic network with SOPs

```
abc 10> read 4bitadder.blif
Hierarchy reader flattened 4 instances of logic boxes and left 0 black boxes.
abc 11> strash
abc 12> print_stats
4bitadder          : i/o =   9/   5 lat =   0 and =   40 lev = 12
abc 12> logic
abc 13> print_stats
4bitadder          : i/o =   9/   5 lat =   0 nd =   40 edge =   80 cube =   40 lev = 12
abc 13> █
```