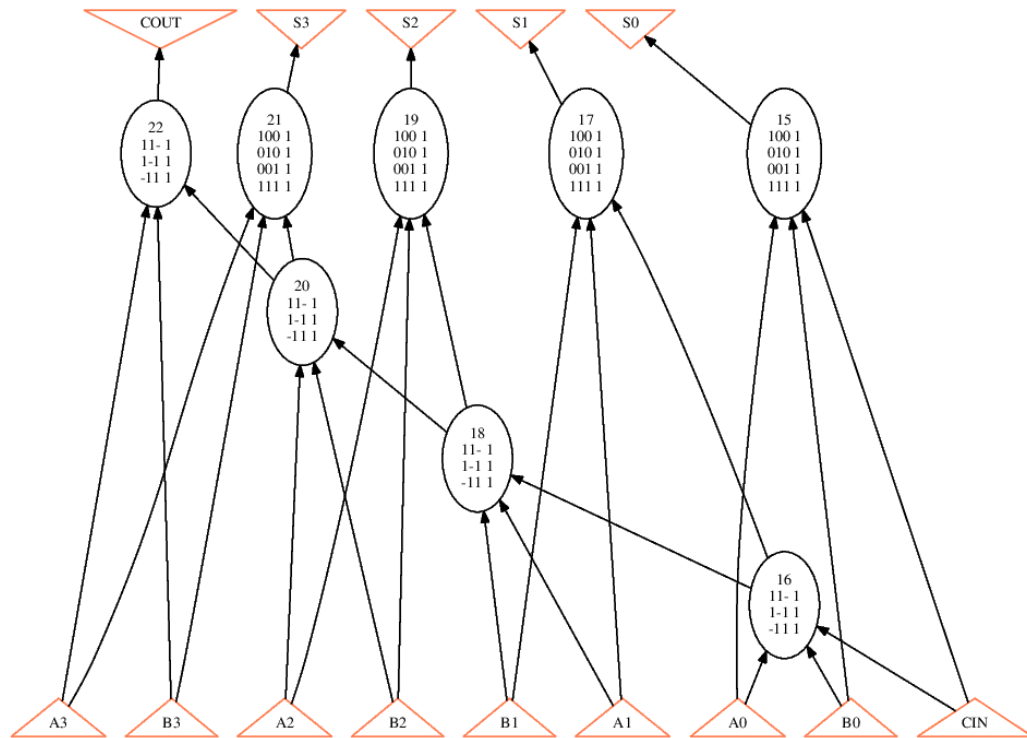


R09943142 邱奕璋

1. visualize the network structure (command show)

Network structure visualized by ABC  
Benchmark "fourbitadder". Time was Tue Oct 13 09:37:22 2020.


The network contains 8 logic nodes and 0 latches.


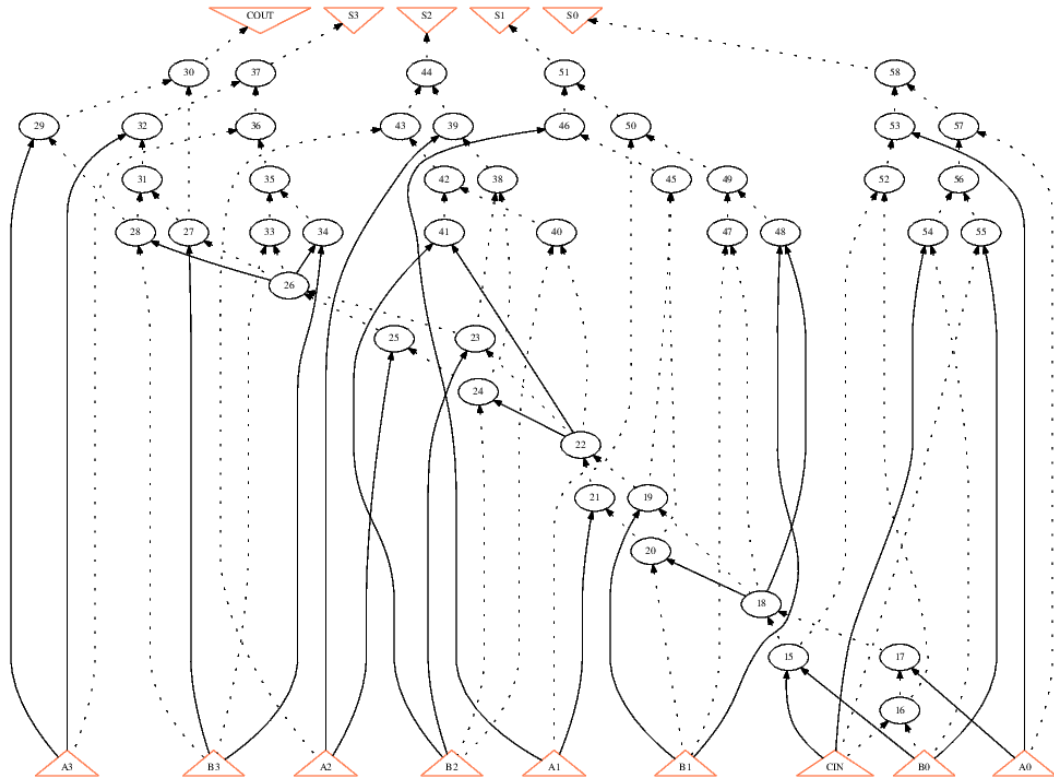
## 2. AIG show

Network structure visualized by ABC  
Benchmark "fourbitadder". Time was Tue Oct 13 09:39:37 2020.

The network contains 44 logic nodes and 0 latches.



### 3. BDD (show\_bdd)

