


I let the four-bit adder input be  $a_0a_1a_2a_3$ , and  $b_0b_1b_2b_3$ . I let the output be four-bit sum  $s_0s_1s_2s_3$  and one-bit carry  $c_3$ .

## Part 1
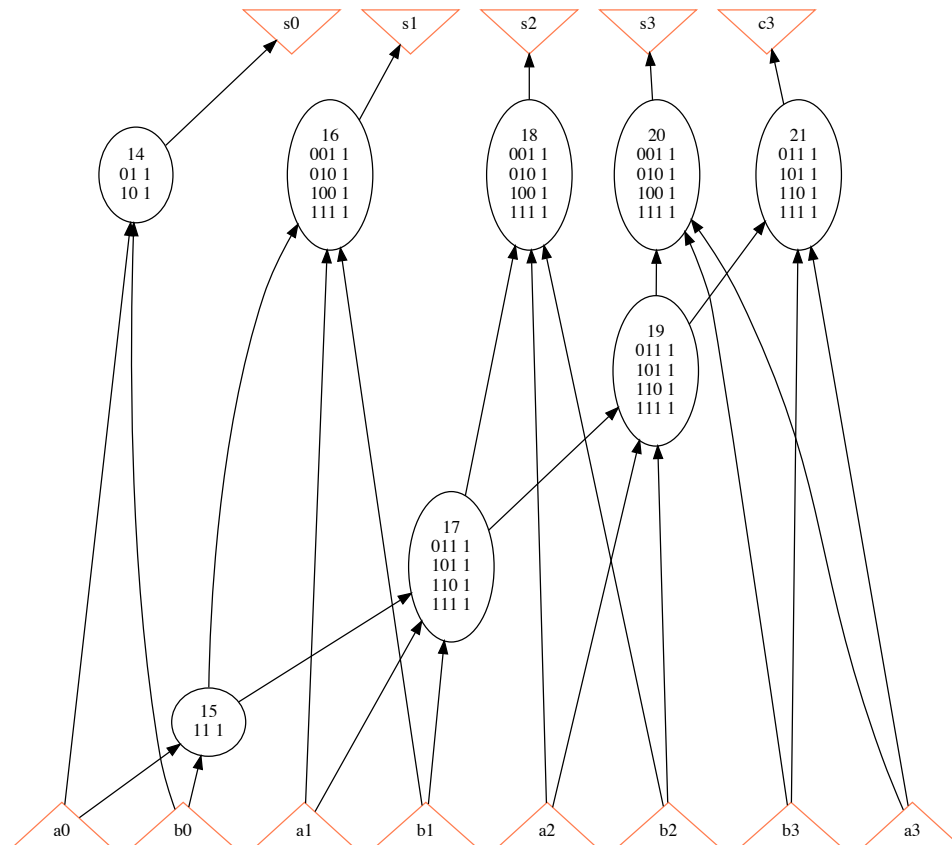
### 1. logic network

Network structure visualized by ABC  
Benchmark "fa4". Time was Wed Oct 14 22:53:03 2020.


The network contains 8 logic nodes and 0 latches.



 
## 2. Strash

Network structure visualized by ABC  
Benchmark "fa4". Time was Wed Oct 14 22:55:59 2020.

The network contains 43 logic nodes and 0 latches.



### 3. Collapse

 

## Part 2

a) Compare the following differences with the four-bit adder example.

1. logic network in AIG (by command `aig`) vs. structurally hashed AIG (by command `strash`)

The information is printed by typing `-h` after the command in `abc`

- “`aig -h`”: converts node functions to AIG. (The entire circuit is still represented by logic network, but the node functions are represented by AIG)
- “`strash -h`”: transforms combinational logic into an AIG. (The entire circuit is represented by AIG)

2. logic network in BDD (by command `bdd`) vs. collapsed BDD (by command `collapse`)

- “`collapse -h`”: collapses the network by constructing global BDDs. (The entire circuit is represented by BDD)
- “`bdd -h`”: converts node functions to BDD. (The entire circuit is still represented by logic network, but the node functions are represented by BDD)

b) Given a structurally hashed AIG, find a sequence of ABC command(s) to convert it to a logic network with node function expressed in sum-of-products (SOP).

- The command “`logic -h`”: Given a structurally hashed AIG, find a sequence of ABC command(s) to convert it to a logic network with node function expressed in sum-of-products (SOP).