

Image of show Aig

Network structure visualized by ABC
Benchmark "4bit_adder". Time was Tue Oct 13 19:36:45 2020.

The network contains 8 logic nodes and 0 latches.

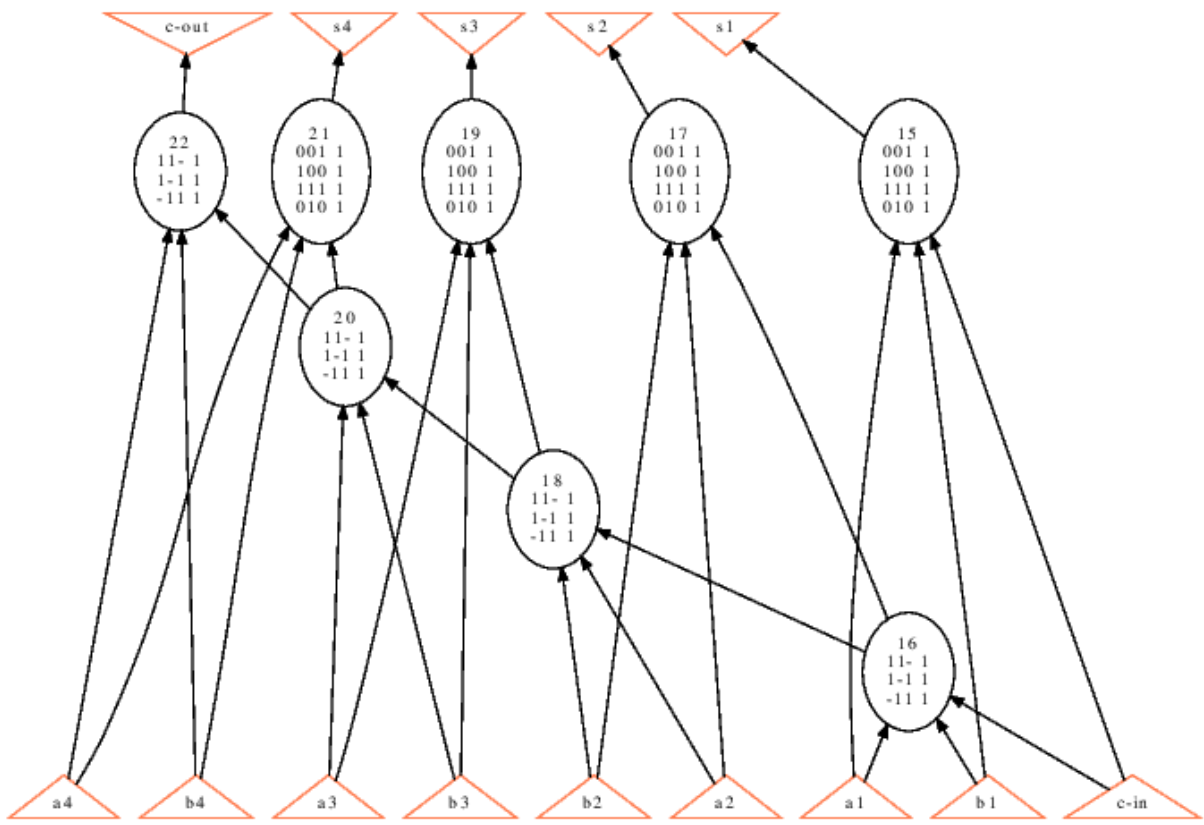


Image of strash

Network structure visualized by ABC
Benchmark "4bit_adder". Time was Tue Oct 13 21:13:41 2020.

The network contains 44 logic nodes and 0 latches.

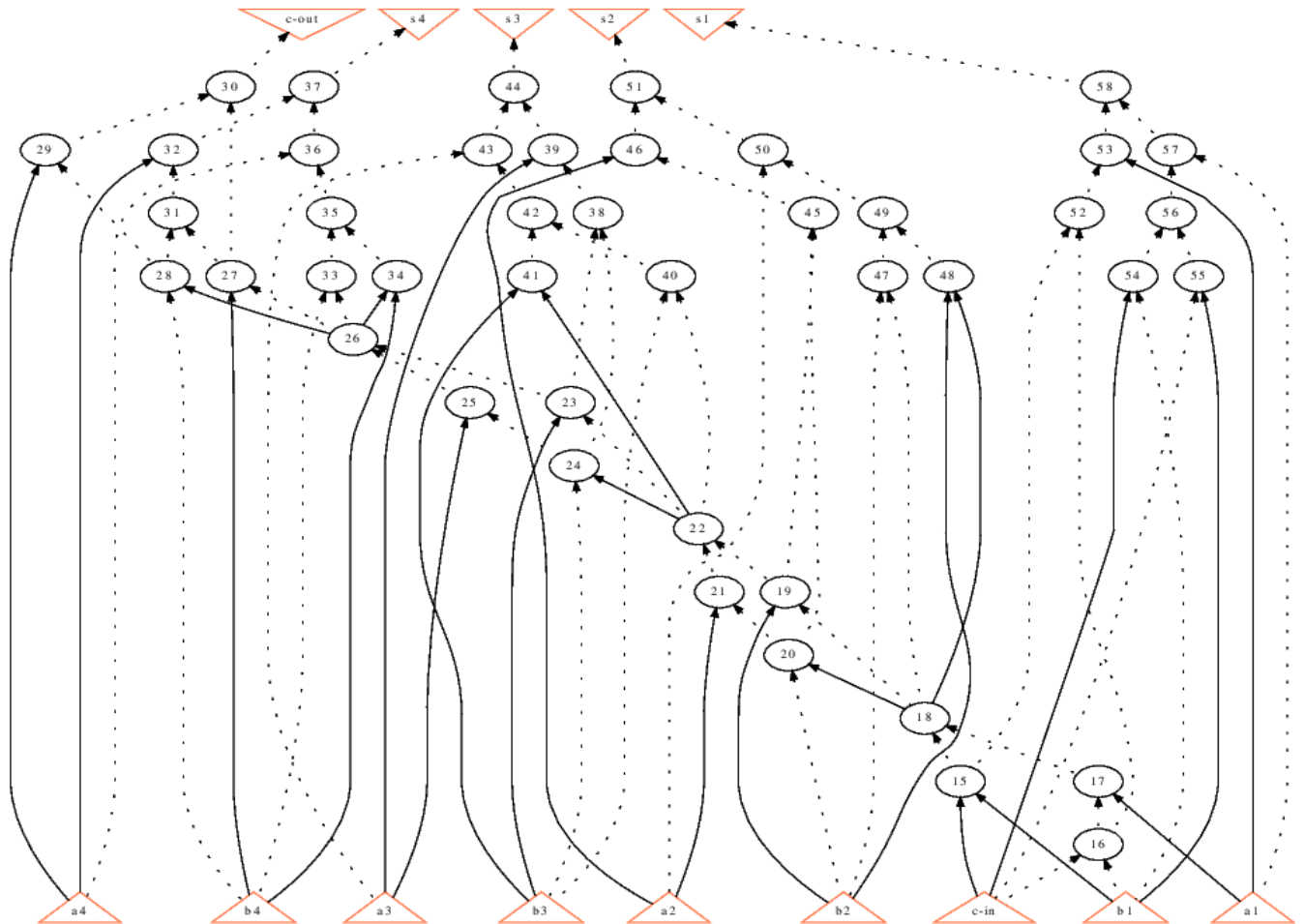


Image of show_bdd

