

LSV PA1


R09943107 陳淳


Part 1.

[show](#)

Network structure visualized by ABC
Benchmark "4bitadder". Time was Thu Oct 15 03:04:32 2020.

The network contains 12 logic nodes and 0 latches.

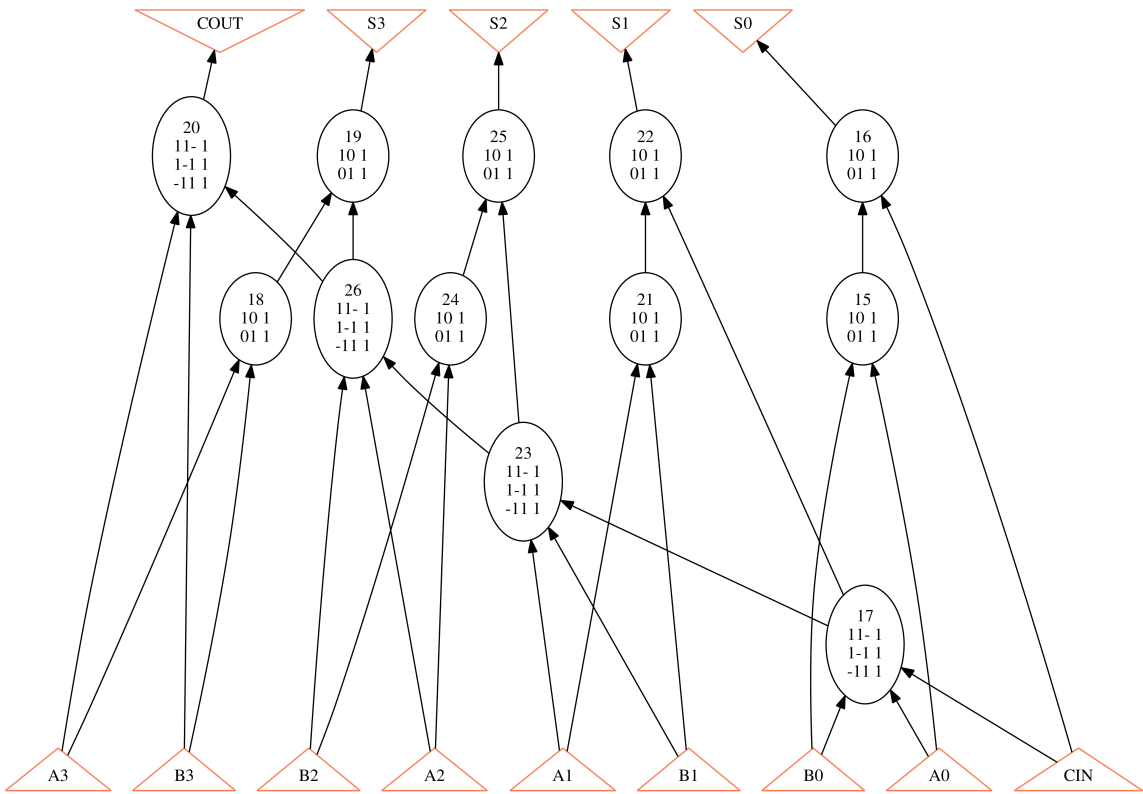

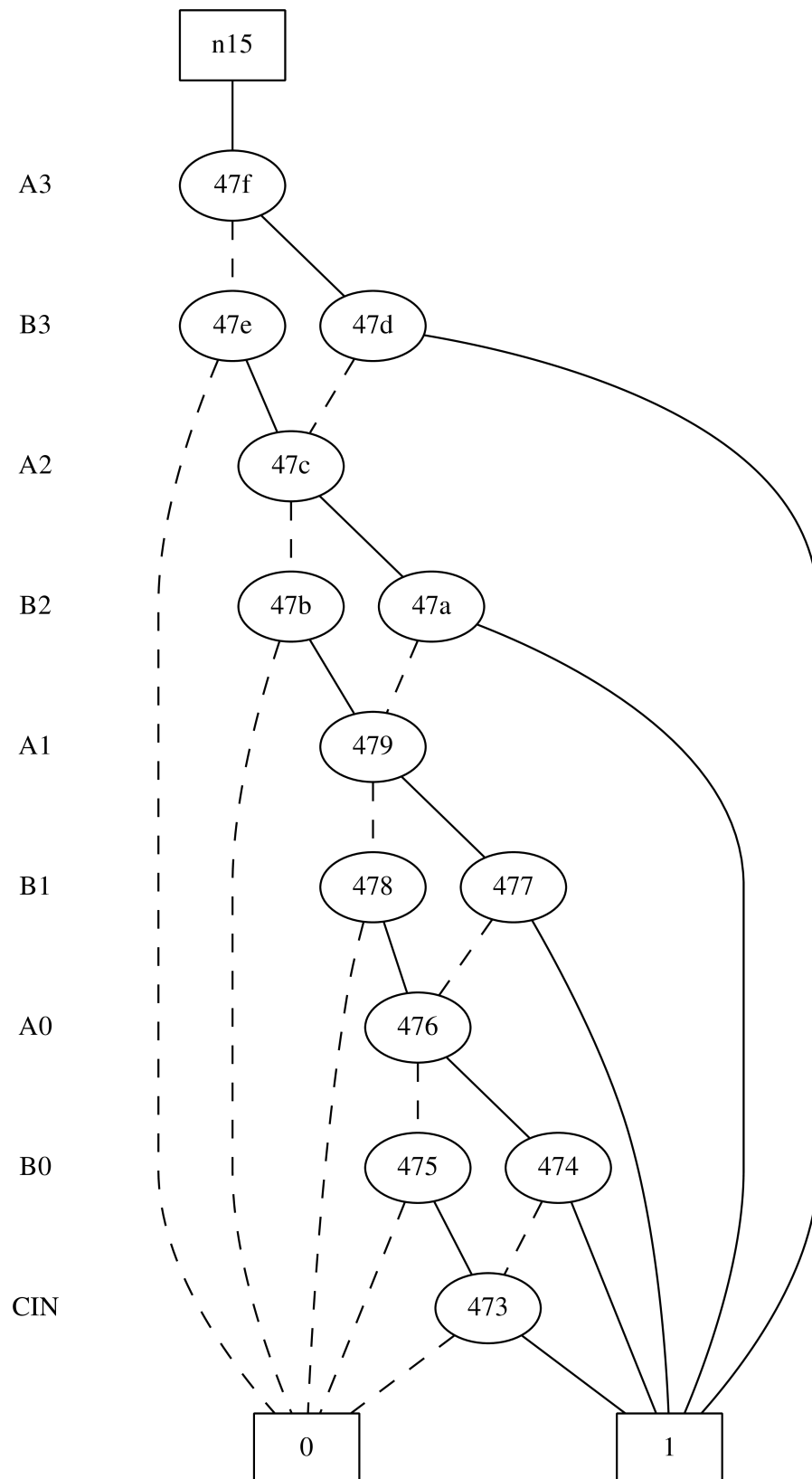

Part 2.

(a) Compare the following differences with the four-bit adder example

Initial `print_stats` on 4bitadder:

```
4bitadder      : i/o =    9/    5  lat =    0  nd =    12  edge =    28
cube =    28  lev = 4
```

1. logic network in AIG (by command `aig`) vs. structurally hashed AIG (by command `strash`)

- `aig`: As the name of the command, it changes the logic network represent method to AIG. But if you use `show` to take a look at the function, you would found that the figure doesn't change.
- `strash`: This command also produced AIG, but it transform the network by one-level structural hashing. Unlike `aig`, the AIG that `strash` produced is represented by 2-input AND gate and its complemented attributes on the edges.

After executing `aig` on 4bitadder, the `print_stats` shows:

```
4bitadder      : i/o =    9/    5  lat =    0  nd =    12  edge =    28
aig  =    40  lev = 4
```

After executing `strash` on 4bitadder, the `print_stats` shows:

```
4bitadder      : i/o =    9/    5  lat =    0  and =    40  lev = 12
```

In `aig`, we can clear see that it has 40 `aig` and 28 `edge`. And in `strash`, we can see that `lev` becomes bigger, and there's no `aig` attributes but 40 `and`.

2. logic network in BDD (by command `bdd`) vs. collapsed BDD (by command `collapse`)

- `bdd`: As the name of the command, it changes the logic network represent method to BDD. But if you use `show` to take a look at the function, you would found that the figure doesn't change.
- `collapse`: Different from `bdd`, though `collapse` also represented the function by BDD in the end, it COLLAPSE the logic network to one-level only. So from CI to CO, it would only has one node in its path.

After executing `bdd` on 4bitadder, the `print_stats` shows:

```
4bitadder      : i/o =    9/    5  lat =    0  nd =    12  edge =    28
bdd  =    32  lev = 4
```

After executing `collapse` on 4bitadder, the `print_stats` shows:

```
4bitadder      : i/o =    9/    5  lat =    0  nd =    5  edge =    33
bdd  =    43  lev = 1
```

We found that **lev** becomes 1 in **collapse**, and it has more **edge** and **bdd** than **bdd**.

(b) Given a structurally hashed AIG, find a sequence of ABC command(s) to covert it to a logic network with node function expressed in sum-of-products (SOP).

To convert AIG to SOP expressed logic network, we can convert it to strashed AIG first, then we can use **logic** command to produce SOP:

```
strash;
logic;
```