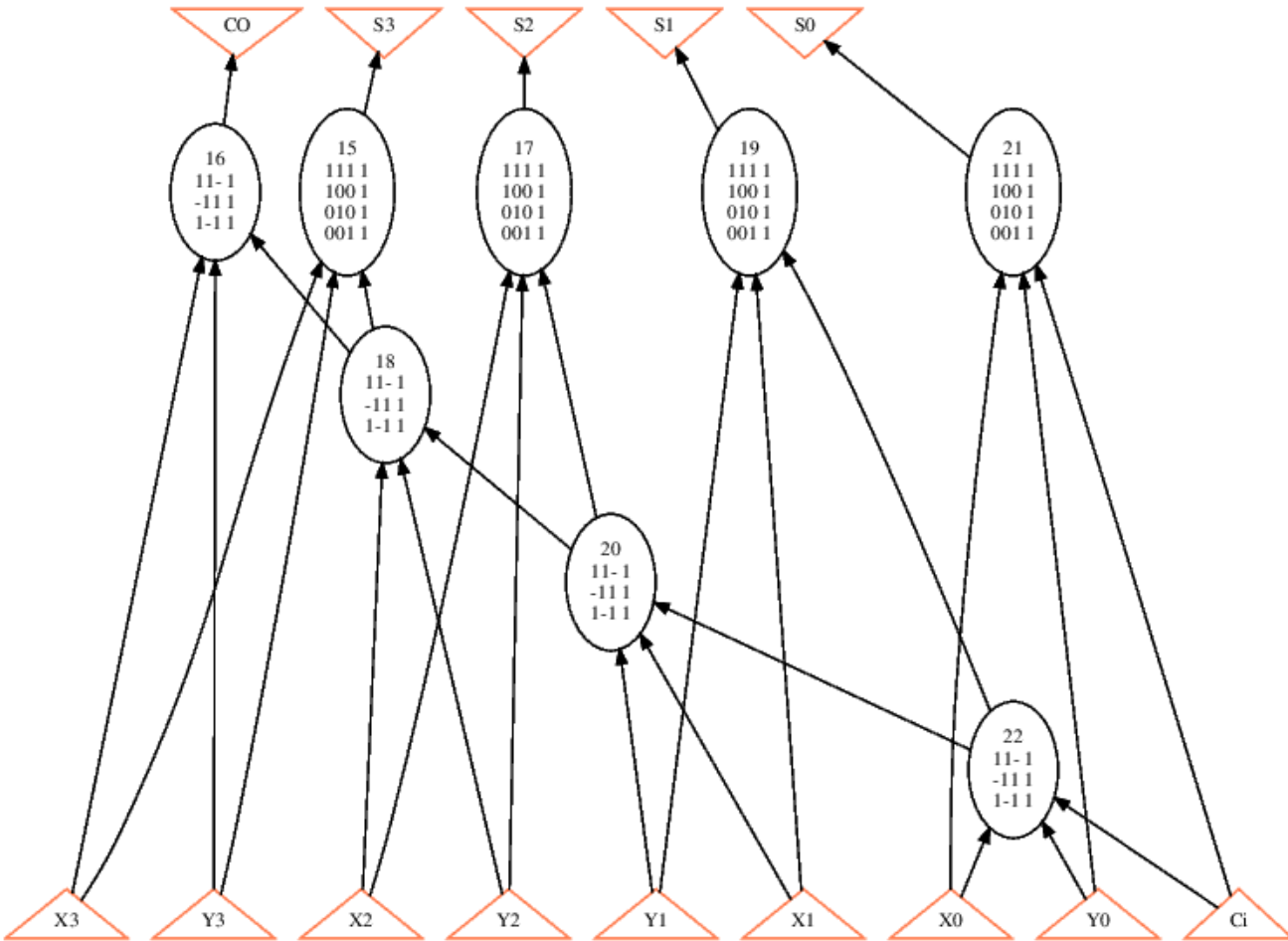



FA4.blif
SOP logic format

Network structure visualized by ABC
Benchmark "FA4". Time was Wed Oct 7 21:01:25 2020.

The network contains 8 logic nodes and 0 latches.





AIG format

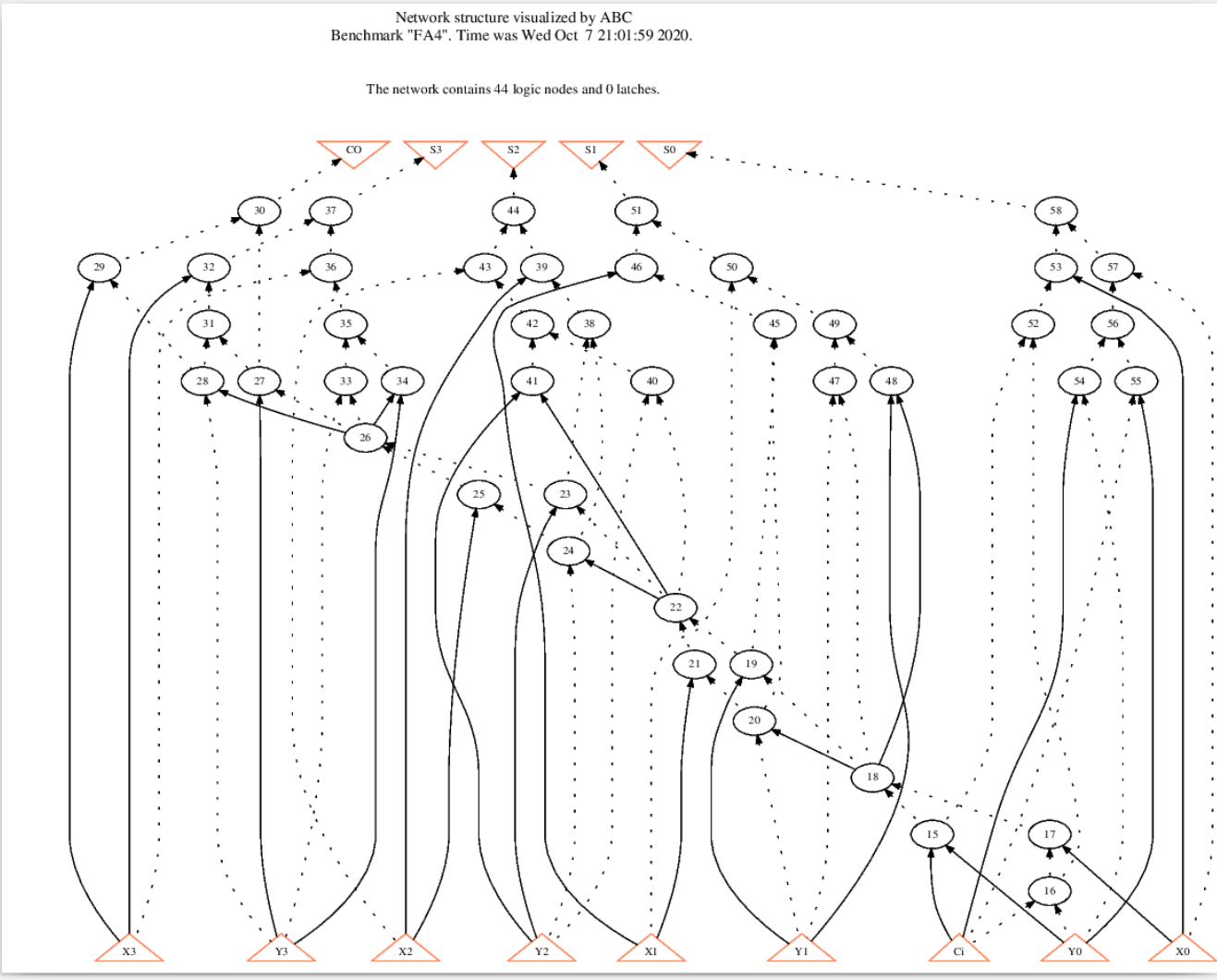


BDD format


CO

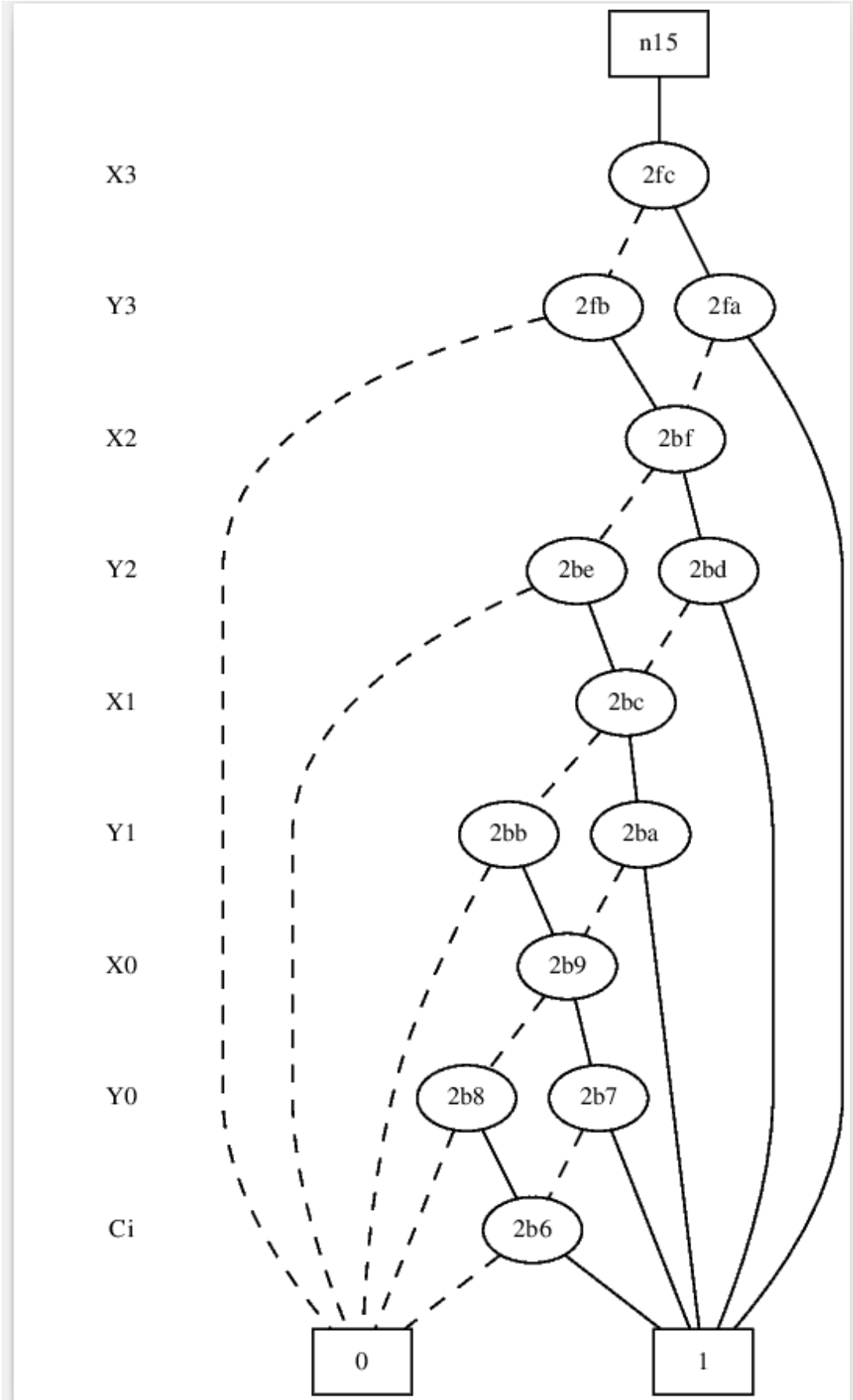

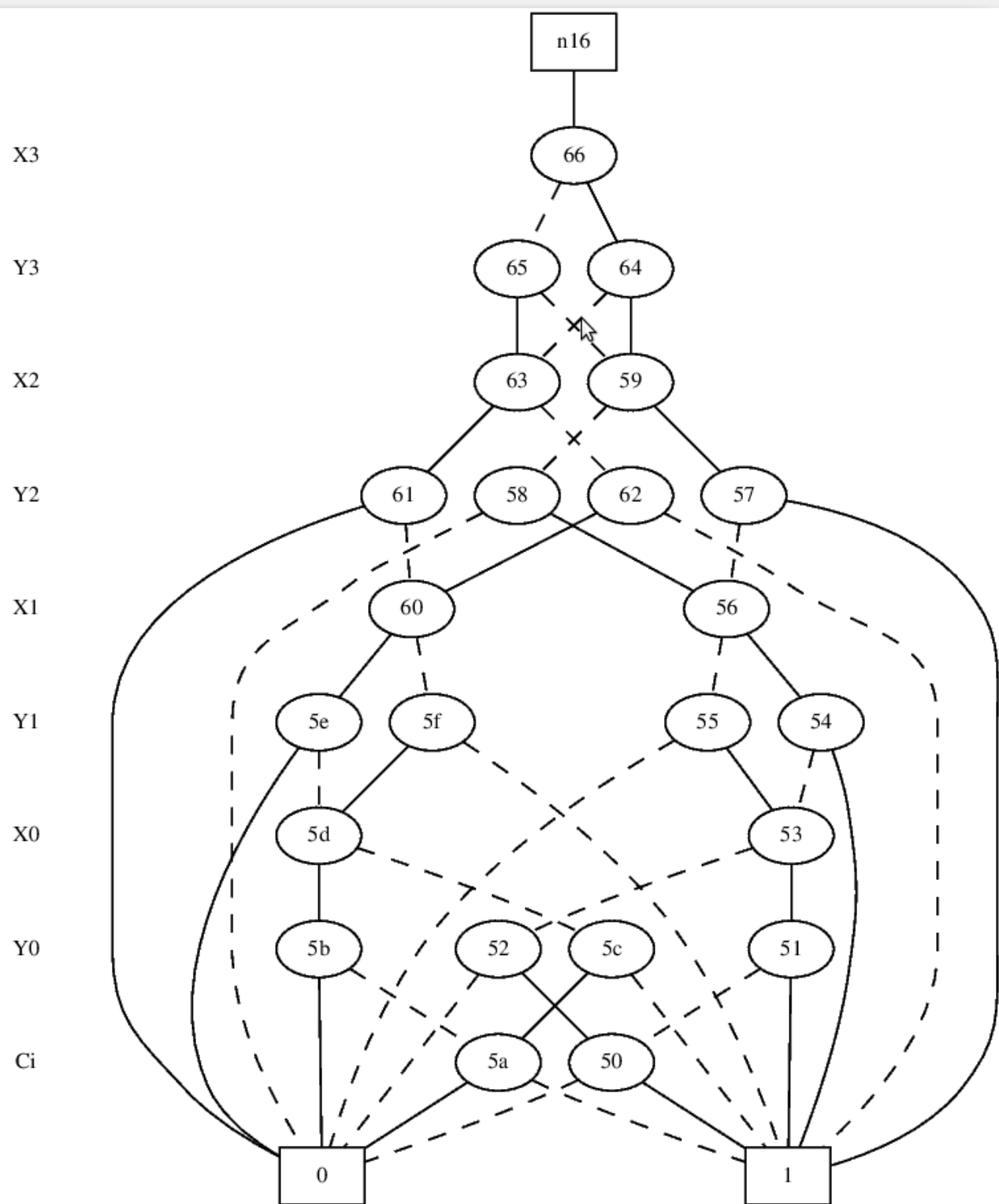

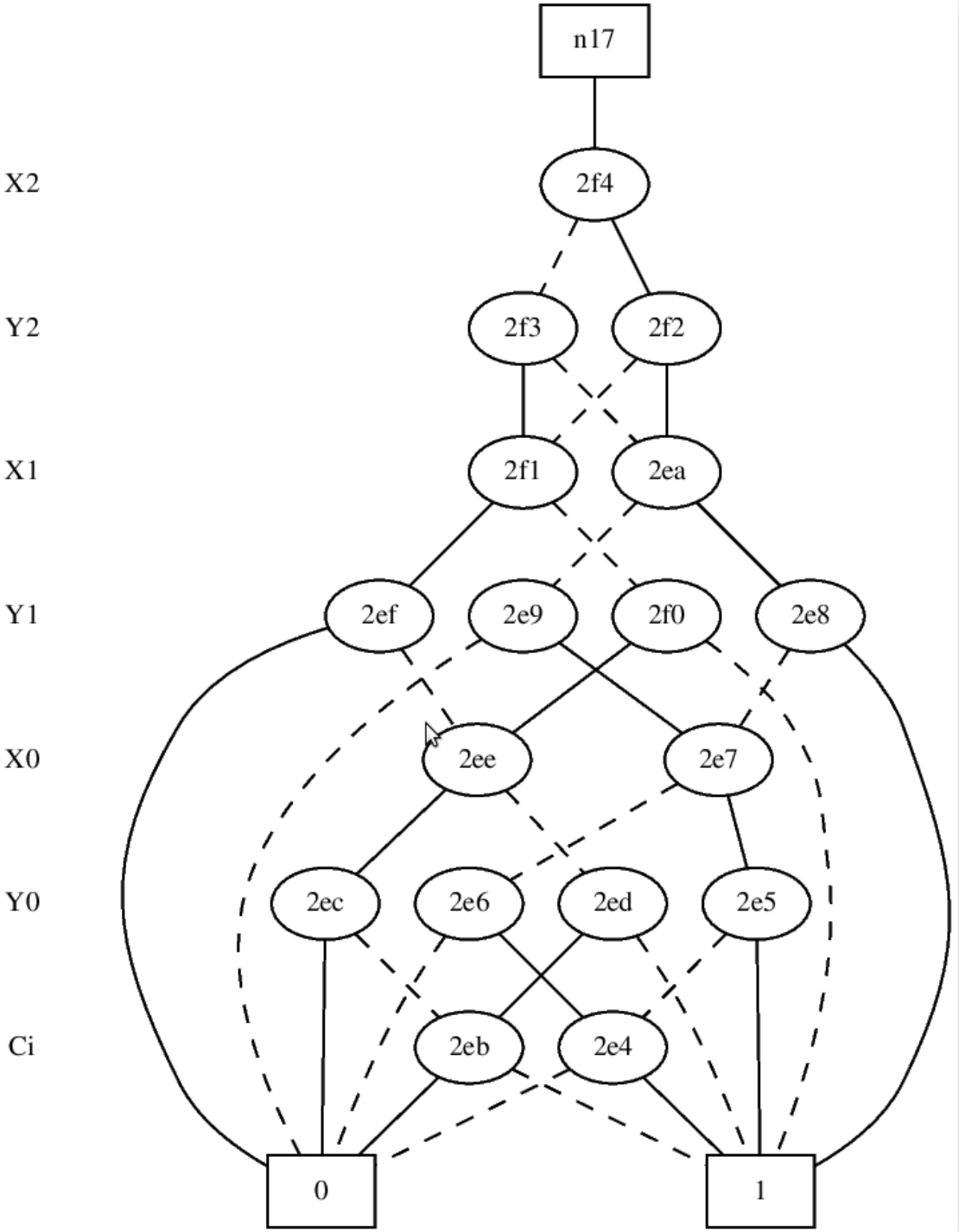

S1

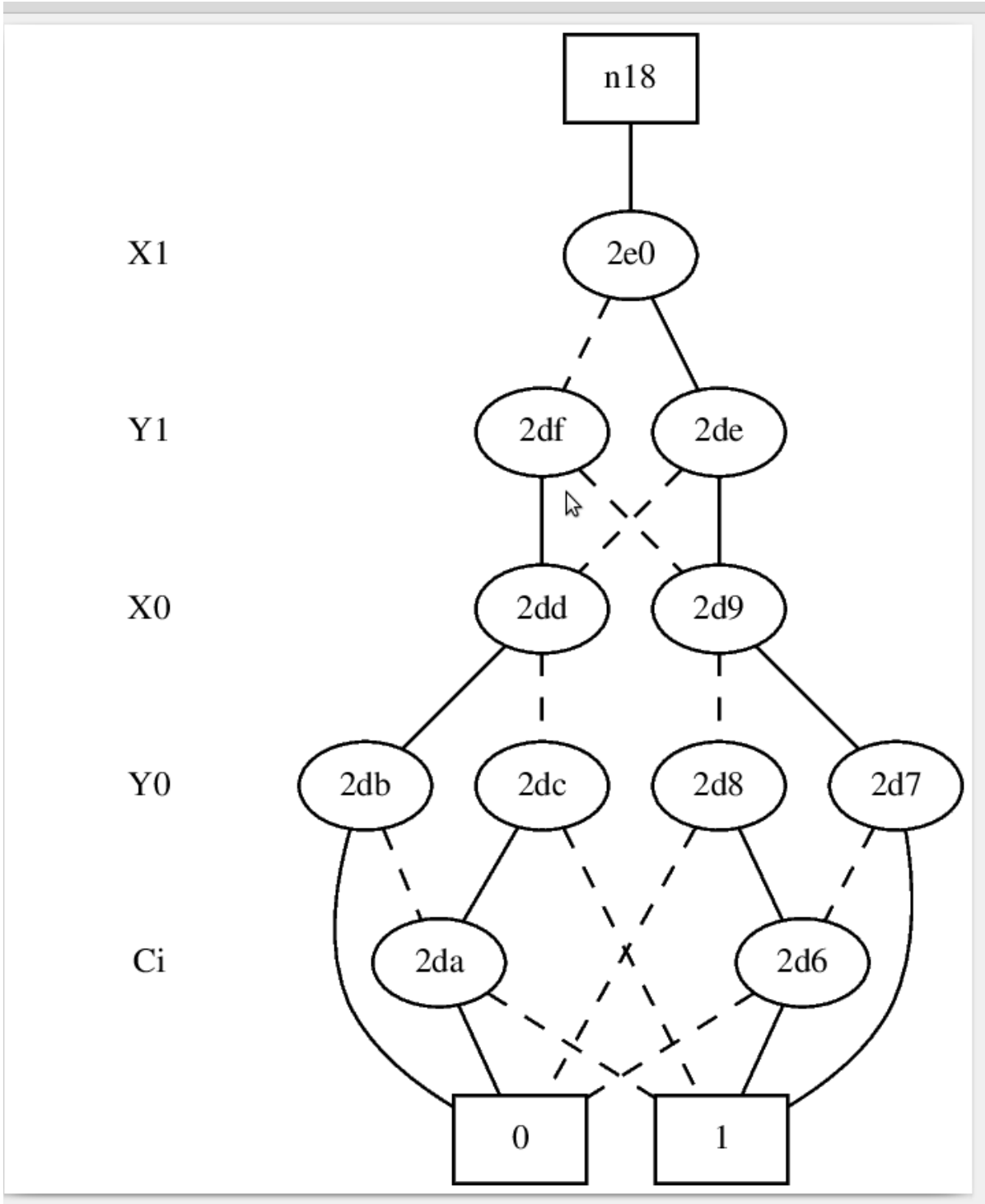

S0

